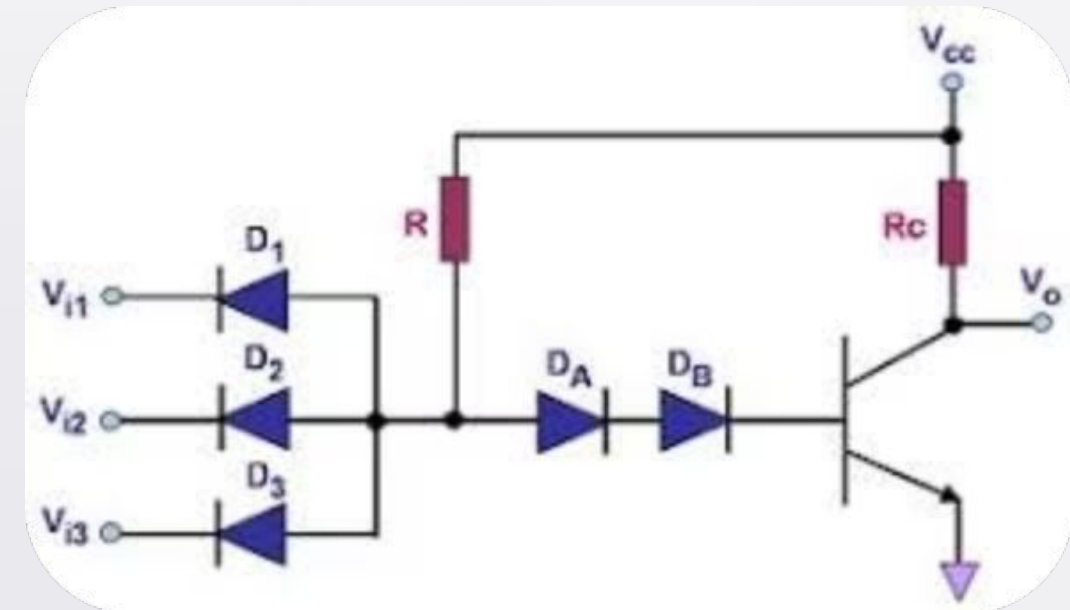


ODARI K. CHARLES

E021-01-1038/2023


Simulation of DTL NAND Gate: Diode Effects and Noise Analysis

Exploring the impact of component modifications in a basic DTL NAND gate




DTL NAND GATE ANALYSIS

schematic Diagram

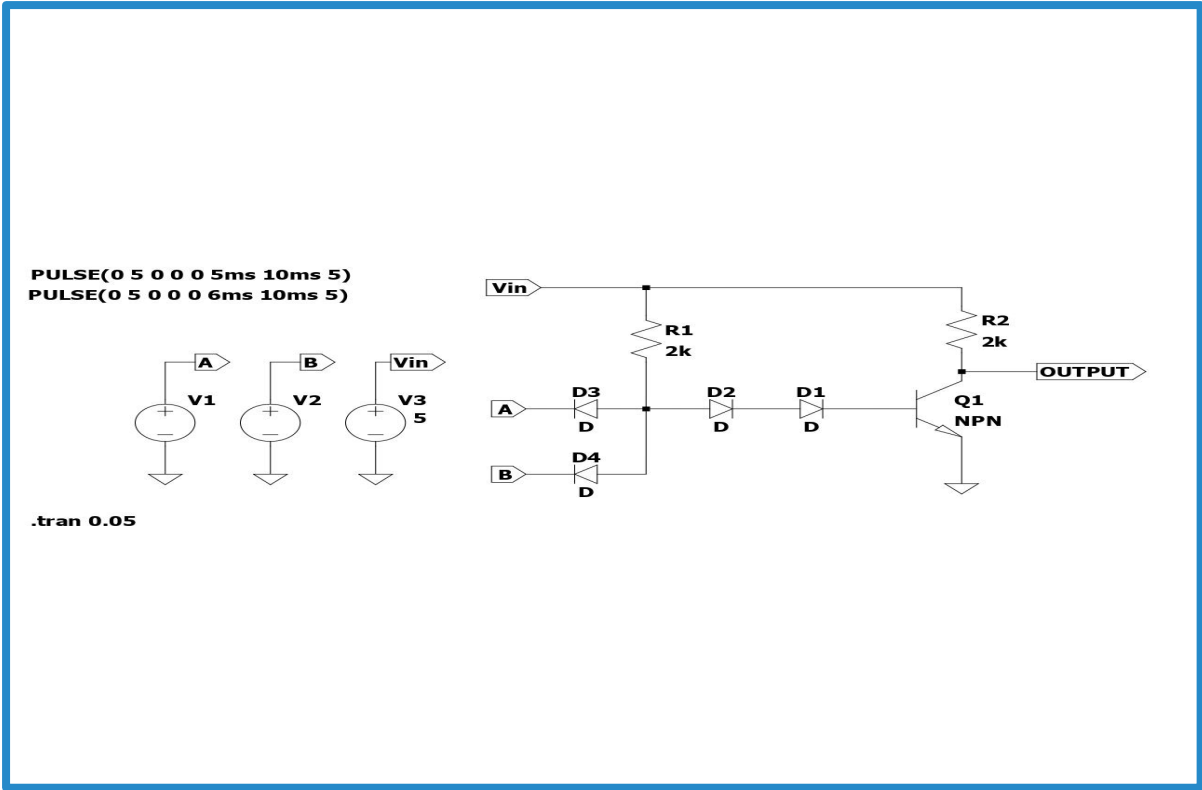

simulation Results


 


Truth Table

A	B	F
0	0	1
0	1	1
1	0	1
1	1	0

Output LOW only if **both inputs are HIGH**

Effect of Removing Diodes & Noise

  

Remove middle 2 diodes

Output logic fails (always **HIGH** or **unstable**).

Inserting D3 and additive noise of 0.9v

The output is partially stable.

Inserting D4 and D3 and additive noise of 0.9v

The output of the DTL NAND gate is stable.

